

# I N T R O D U C T I O N


# Outline

- Review Basic Computer of System Architecture I
- Introduce Pico-processor
- Memory Access Cycle
- Input/Output Instructions


# Introduction: the Pico-Processor

- Objective
  - Simple design of a processor
  - Executes a few simple instructions
  - Gain understanding of processor hardware principles
- Basic idea
  - Processor is basically a collection of digital logic components

# Basic Computer Architecture

 


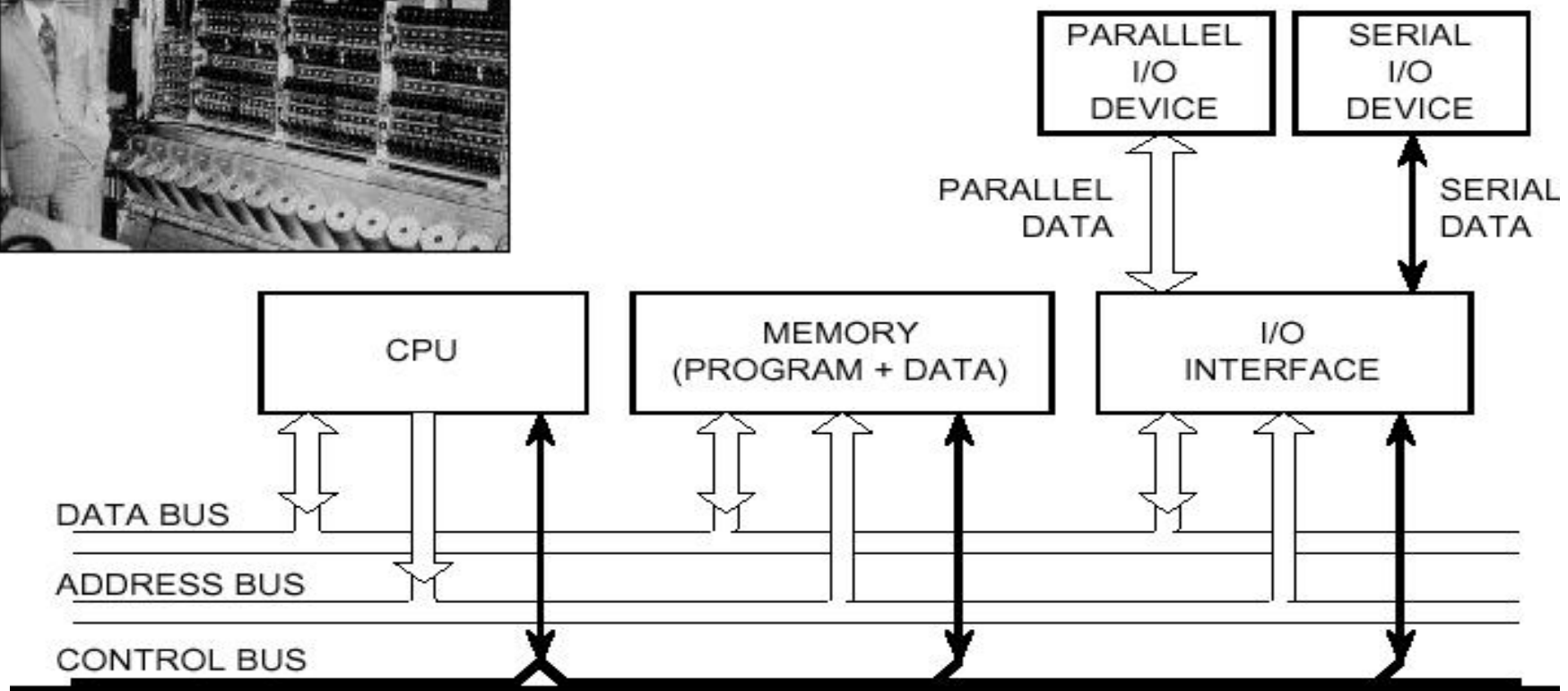*Based on von Neumann architecture Developed in 1945*


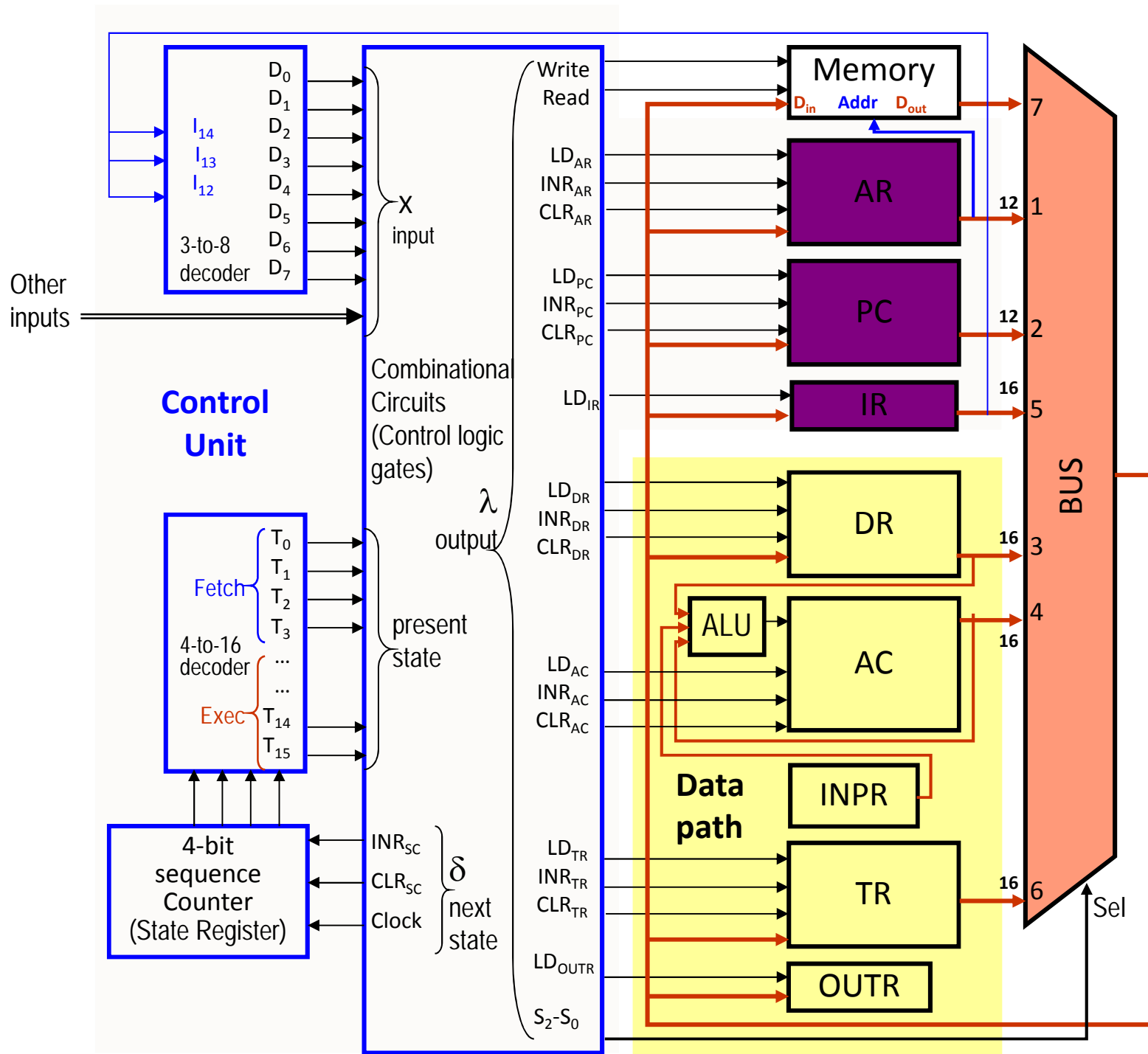
# Computer Architecture I – Reminder


- Basic Computer
  - 8 General purpose Register
    - ✓ Support Load, Reset, Increment
  - 16 bit common data bus
  - 12 bit address bus
  - $2^{12} = 4096$  word memory space = 4096 x 16 bit
  - Complete instruction set architecture
    - ✓ Data manipulation
    - ✓ Program flow
    - ✓ Input/output




# BASIC COMPUTER
 
# Basic Computer Instruction Set


- There are three types of instructions which have different formats:
- **Memory Reference Instruction** – MRI
  - Direct Addressing ( $I=0$ )
  - Indirect Addressing ( $I=1$ )
- **Register Reference Instruction** - RRI
- **Input-Output Instruction** - IOI



(a) Memory – reference instruction

 

(b) Register – reference instruction

 

(c) Input – output instruction

Symbol	I=0	I= 1	Description
<b>MRI</b>			
<b>AND</b>	0xxx	8xxx	AND memory word to AC
<b>ADD</b>	1xxx	9xxx	Add memory word to AC
<b>LDA</b>	2xxx	Axxx	Load memory word to AC
<b>STA</b>	3xxx	Bxxx	Store content of AC in memory
<b>BUN</b>	4xxx	Cxxx	Branch unconditionally
<b>BSA</b>	5xxx	Dxxx	Branch and save return address
<b>ISZ</b>	6xxx	Exxx	Increment and skip if zero
<b>RRI</b>			
<b>CLA</b>	7800		Clear AC
<b>CLE</b>	7400		Clear E
<b>CMA</b>	7200		Complement AC
<b>CME</b>	7100		Complement E
<b>CIR</b>	7080		Circulate right AC and E
<b>CIL</b>	7040		Circulate left AC and E
<b>INC</b>	7020		Increment AC
<b>SPA</b>	7010		Skip next instruction if AC positive
<b>SNA</b>	7008		Skip next instruction if AC negative
<b>SZA</b>	7004		Skip next instruction if AC zero
<b>SZE</b>	7002		Skip next instruction if E is 0
<b>HLT</b>	7001		Halt computer
<b>IOI</b>			
<b>INP</b>		F800	Input character to AC
<b>OUT</b>		F400	Output character from AC
<b>SKI</b>		F200	Skip on input flag
<b>SKO</b>		F100	Skip on output flag
<b>ION</b>		F080	Interrupt on
<b>IOP</b>		F040	Interrupt off

# BASIC COMPUTER



# Instruction Set Completeness

- A computer instruction set is complete if it can be used to evaluate any function that is known to be computable.
- To be complete, the instruction set must contain enough instructions in each of the following categories:
  1. Arithmetic, logic, and shift instructions.
  2. Instructions for moving information to and from memory and processor registers. (load/store)
  3. Program control instructions together with instructions that check status conditions.
  4. Input and output instructions

# Instruction Set Completeness


- Program control instructions, such as branch instructions, are used to change the sequence in which the program is executed.
- **Input and output instructions** are needed for communication between the computer and the user (outside world).
- In this context, the instruction list of the Basic Computer is complete as it provides enough instructions in each category.

# Basic Computer Instruction Cycle


- A program residing in the memory of the computer consists of a sequence of instructions. Each instruction is executed in several steps:
  1. Fetch an instruction from memory.
  2. Decode the instruction.
  3. Read the effective address from memory if the instruction has an indirect address.
  4. Execute the instruction.
- Upon the completion of step 4, the control goes back to step 1 to start over the cycle for the next instruction.
- The process is repeated indefinitely unless a **HALT** instruction is encountered.
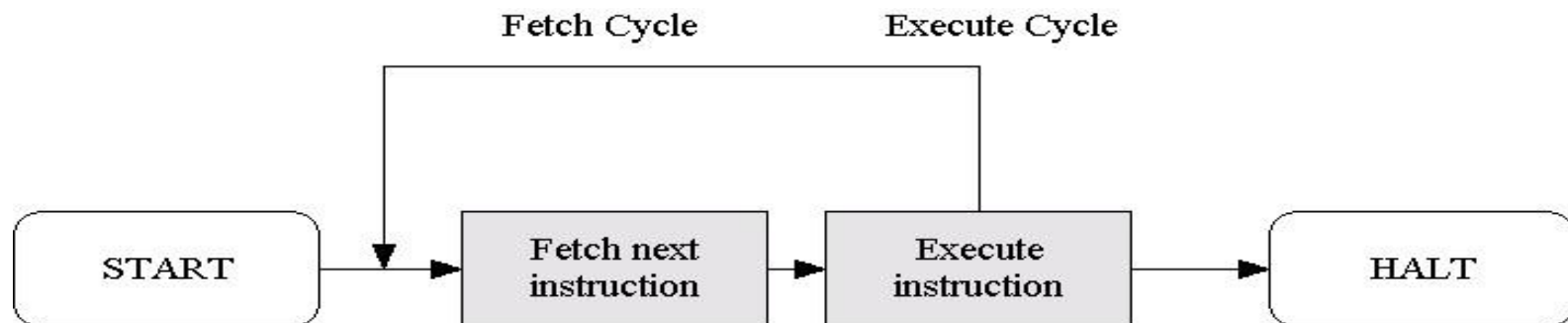
# Basic Instruction Cycle

- Computer performs the instruction cycle forever! (or at least until it is turned off, faces an error or is instructed to STOP)



# Detailed Instruction Cycle

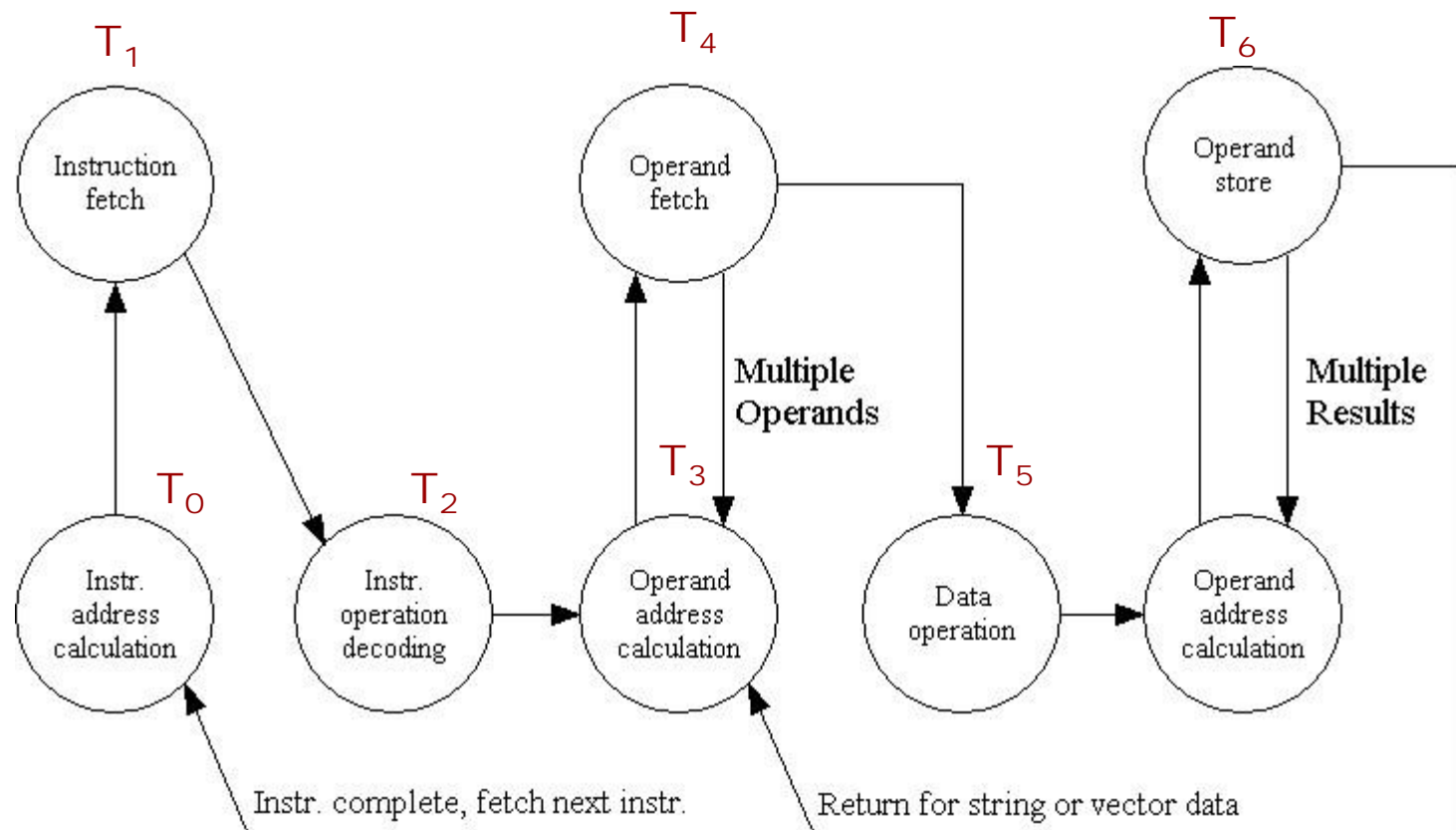

# Detailed Instruction Cycle


- **T0 - Instruction address calculation:** Determines the address of the next instruction to be executed (PC)
- **T1 - Instruction fetch** Reads the instruction from memory location into the processor - IR
- **T2 - Instruction operation decoding** Analyzes the instruction to determine the type of operation to be performed and the operand(s) to be used
- **T3 - Operand address calculation** Determines the operand address (if needed) - AR

# Detailed Instruction Cycle

- T4 - Instruction execution Operand fetch: Fetches the operand from memory or reads it from I/O -> AC
- T5 – Instruction execution Data operation: Performs the operation indicated in the instruction (ALU)
- T6 - Instruction execution Operand store: Write the results into memory or out to I/O
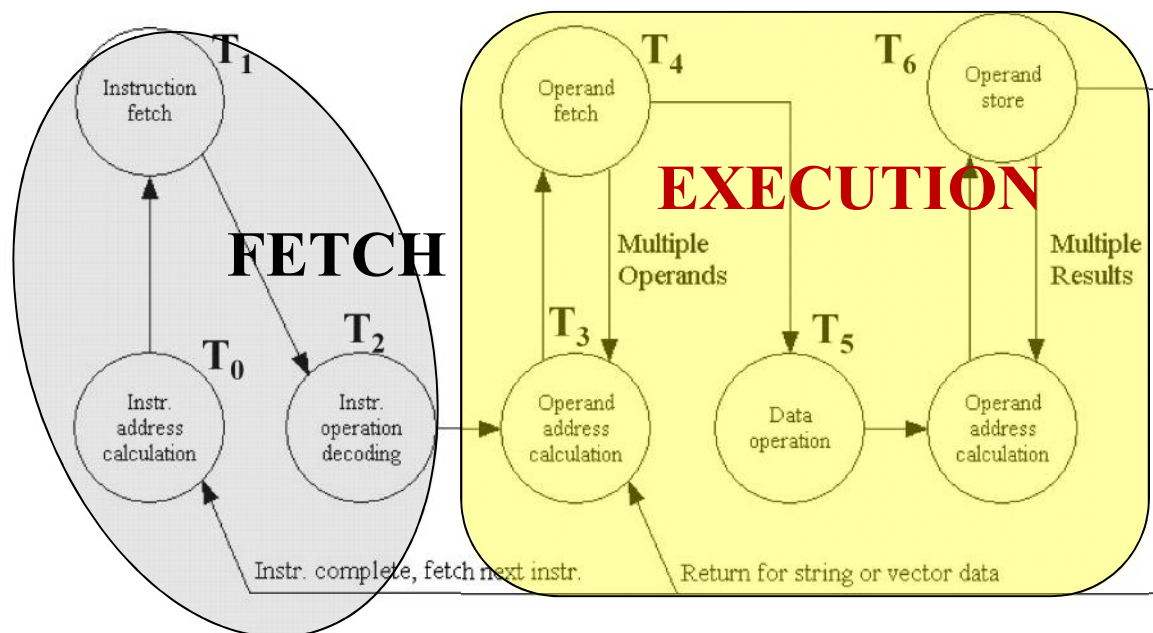
# High Level Division of Instruction Cycle

- We first divide the instruction cycle into 2 major phases: ASM Level1 (High level of detail)
  1. **Fetch** Phase: T0-T2
  2. **Execution** Phase: T3-T6






# Fetch Cycle – @ ASM Level1

- **Fetch** instruction from memory location specified by PC to Instruction Register (IR)
  1.  $T_0: AR \leftarrow [PC]$  - Transfer contents of PC to Memory Address Register
  2.  $T_1: IR \leftarrow [M(AR)]$  - Fetch instruction = contents of addressed memory location  $[M(AR)]$  is transferred to the IR
  3.  $T_1: PC \leftarrow PC + 1$  - PC incremented to point to the next instruction
  4.  $T_2$  Instruction decoded by CU – now that instruction is in IR


Fetch Cycle is concerned with the following registers (highlighted in light blue):

1. AR
2. PC
3. IR

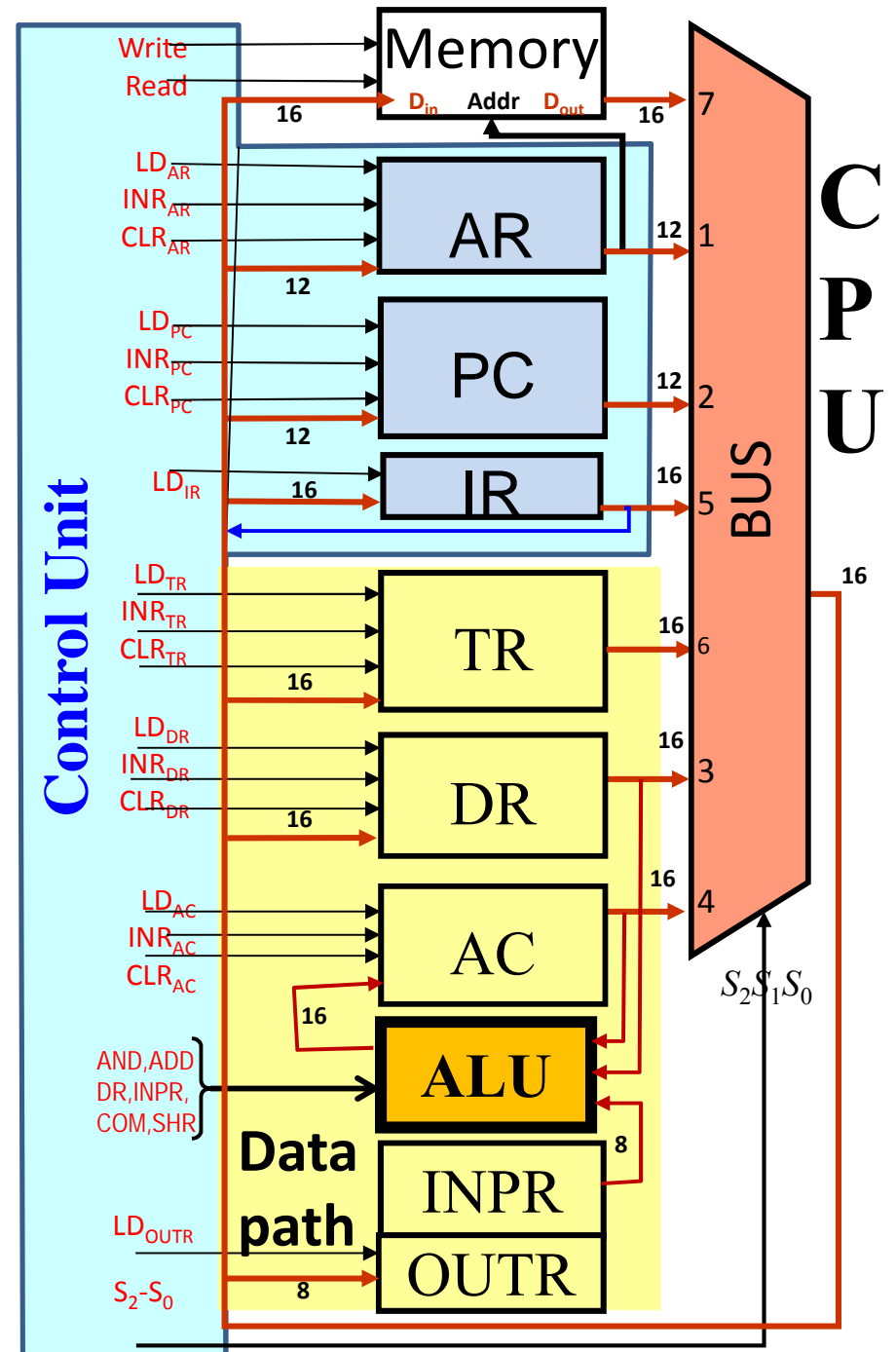

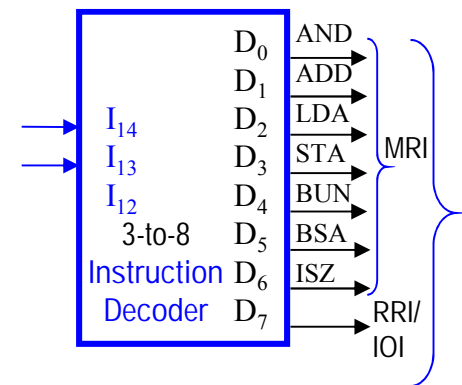
# How Instructions are Decoded?

- Instructions are decoded using the **Instruction Decoder**
  - 3x8 decoder
  - 3bit input: bits [14:12] of the instruction register (IR)
  - 8 bit output: one-hot instruction



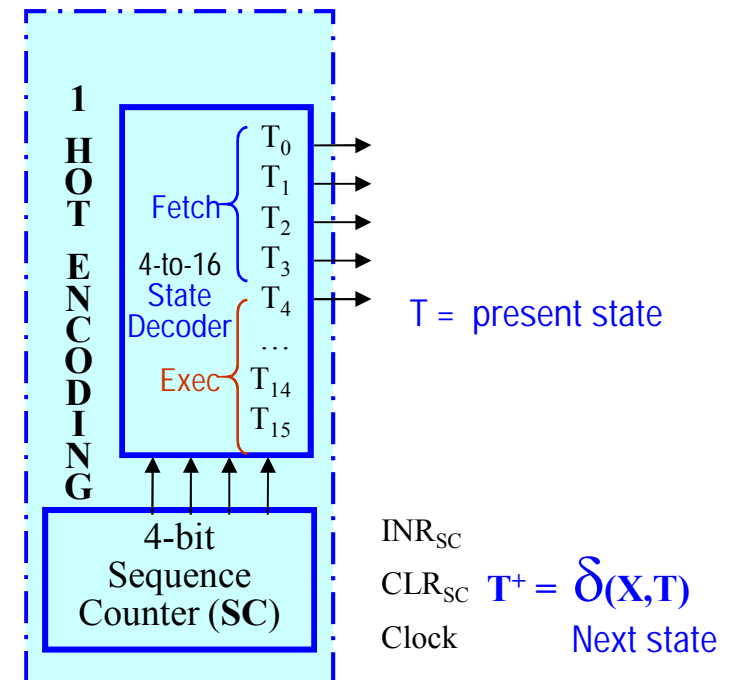
# How is Timing Determined?

- The Control Unit utilizes a 4-bit (modulo 16) counter and 4-to-16 decoder to determine Timing events T<sub>0</sub>-T<sub>15</sub>
  - First few timing events are used by **Fetch cycle**
  - Last few are used by **Exec cycle**



# COMPUTER

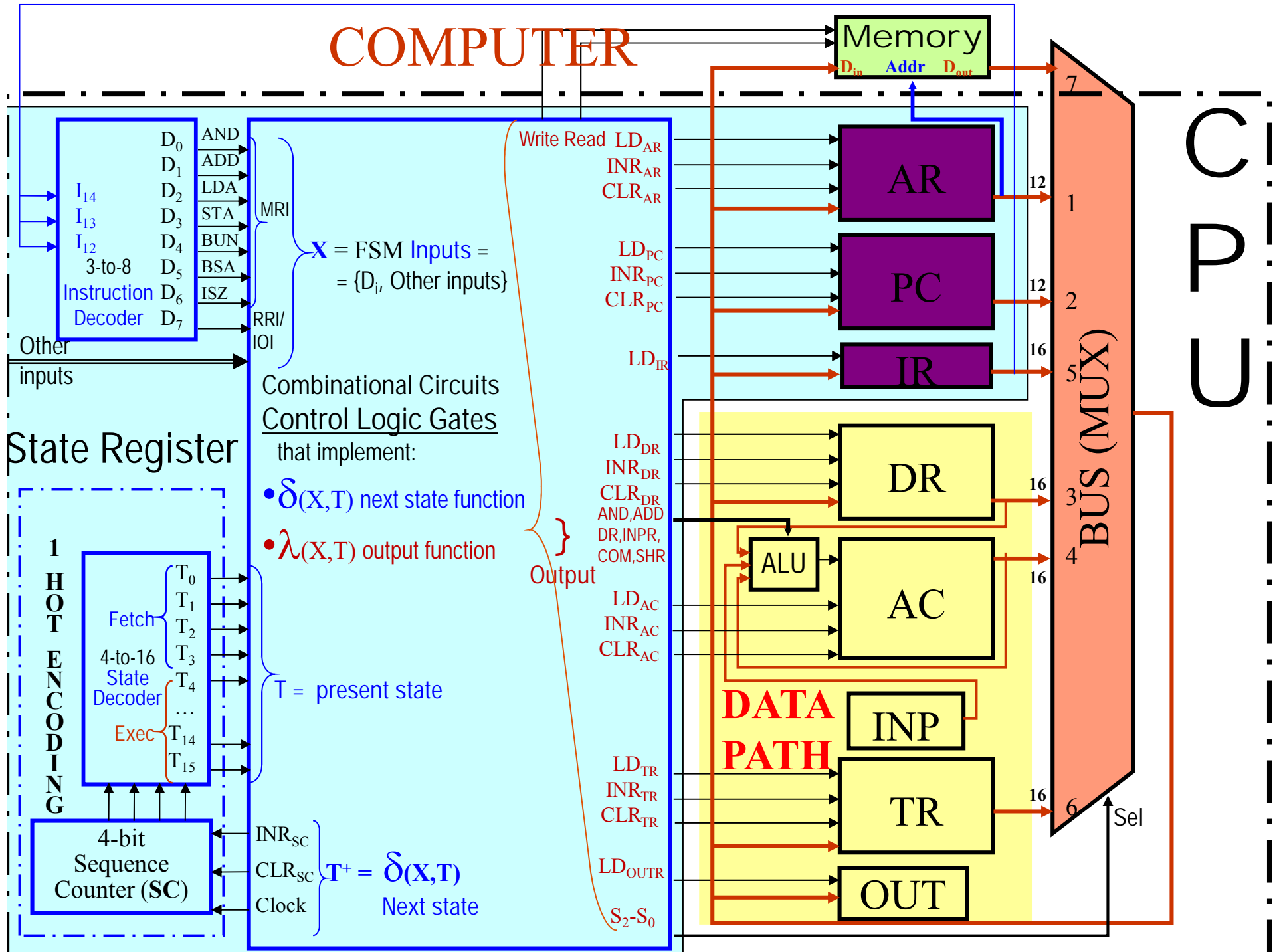


# Pico Controller


- Simple design of a processor
- Executes a few simple instructions
- Processor is basically a collection of digital logic components
  - Arithmetic Unit: support only ADD/SUB
  - 2 Accumulator Registers A & B
  - 8 bit data bus
  - Up to 4 input devices
  - Up to 4 output devices

# Pico Controller Instruction Set

Instruction	Operands	RTL	Instruction Code
ADD	N/A	A    A + B	001XXXXX
SUB	N/A	A    A - B	011XXXXX
IN	Device#, Dest Register	dd    ii	101Xiidd
OUT	Src Register, Device#	oo    ss	111Xssoo
MOV	Src & Dest Registers	dd    ss	010Xssdd

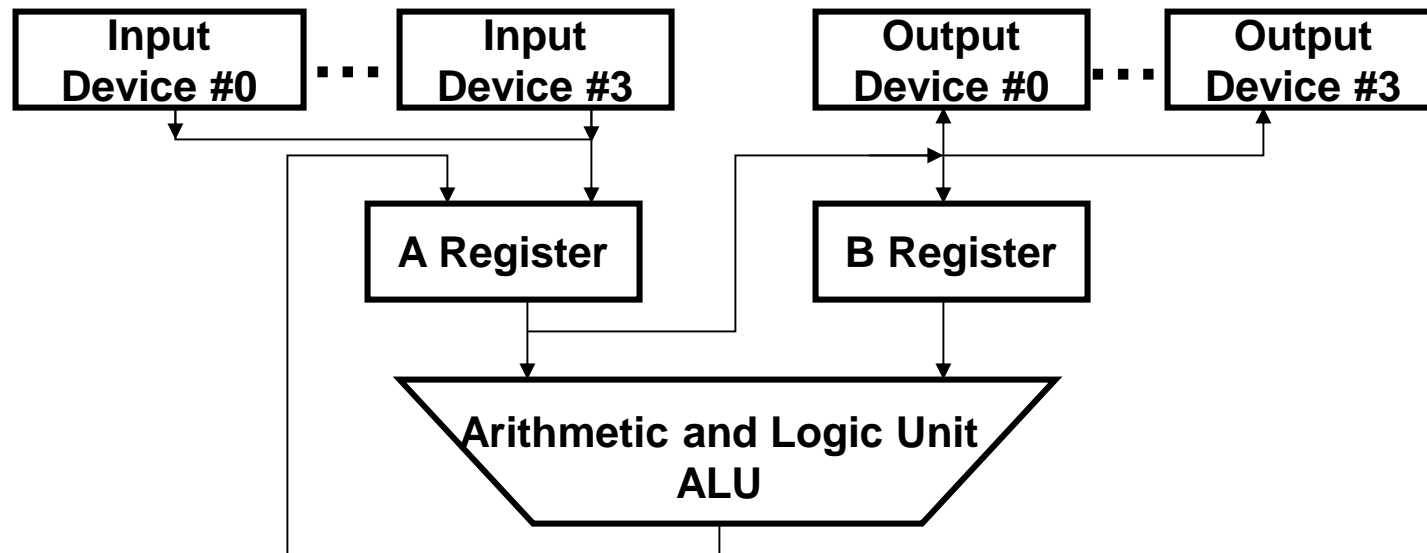

# Computer Memory

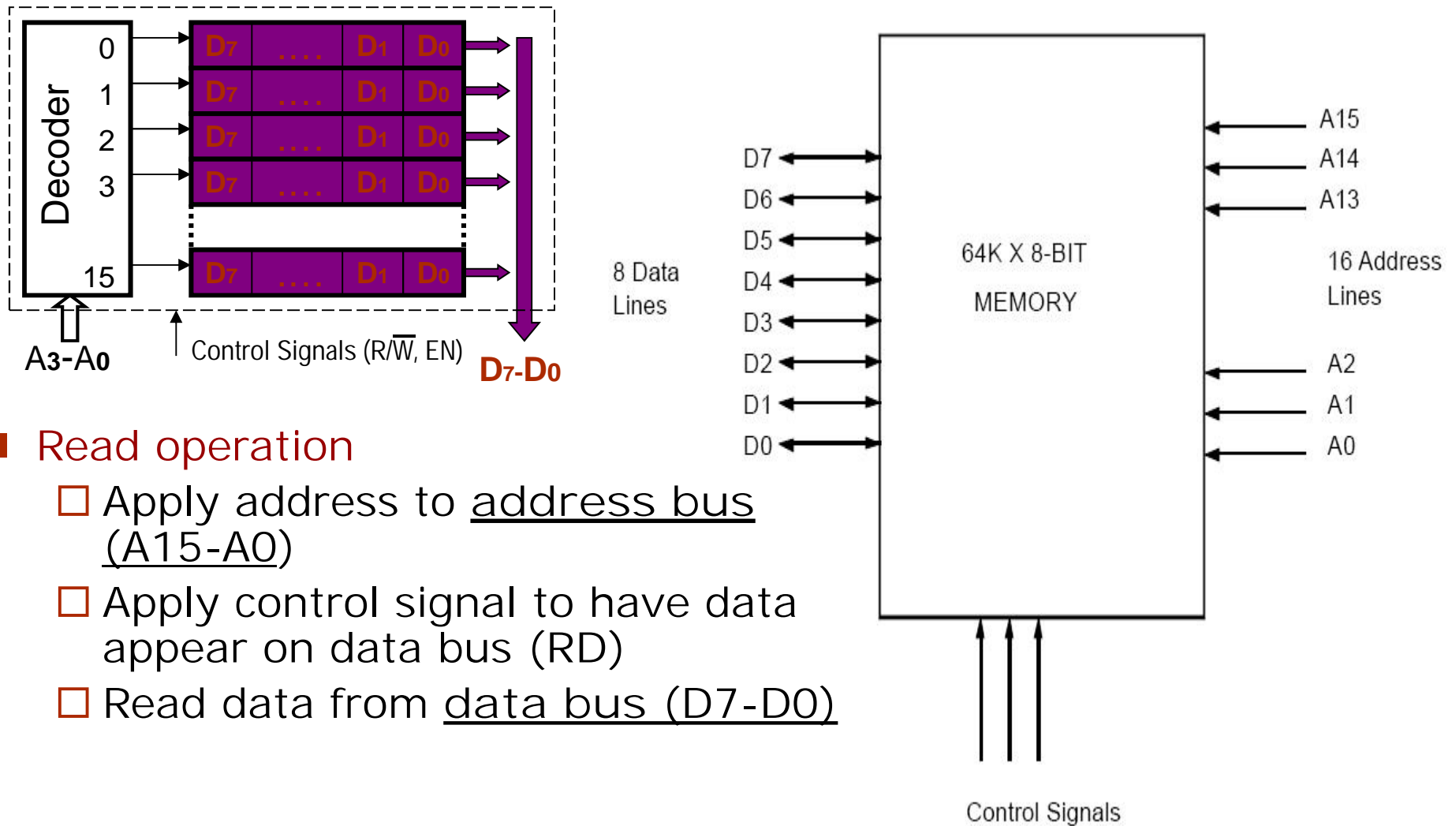


## ■ Read operation

- Apply address to address bus (**A15-A0**)
- Apply control signal to have data appear on data bus (**RD**)
- Read data from data bus (**D7-D0**)




# Computer Memory

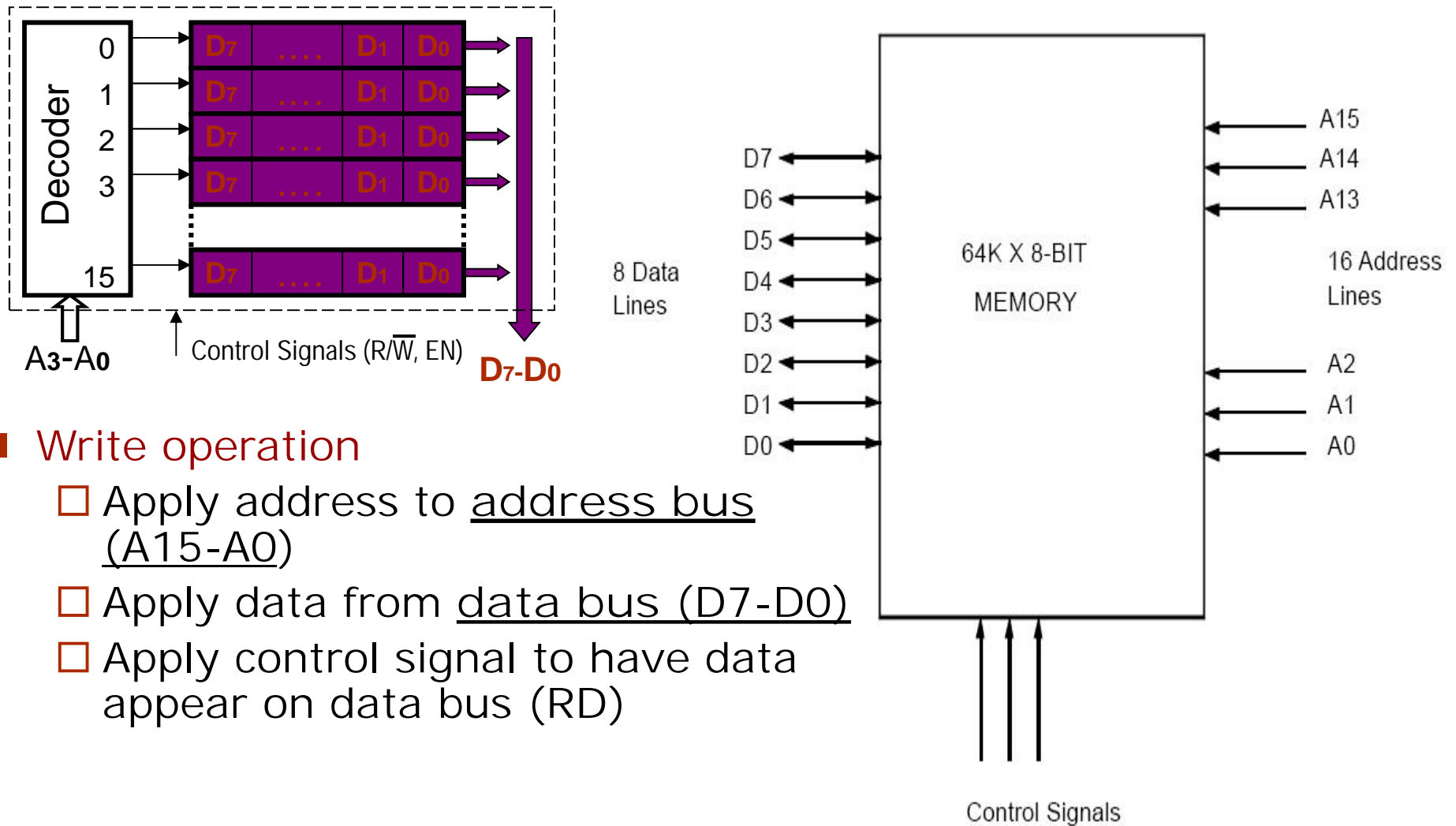

## ■ Write operation

- Apply address to address bus (**A15-A0**)
- Apply data from data bus (**D7-D0**)
- Apply control signal to have data appear on data bus (**RD**)


# Computer Memory – RAM & ROM

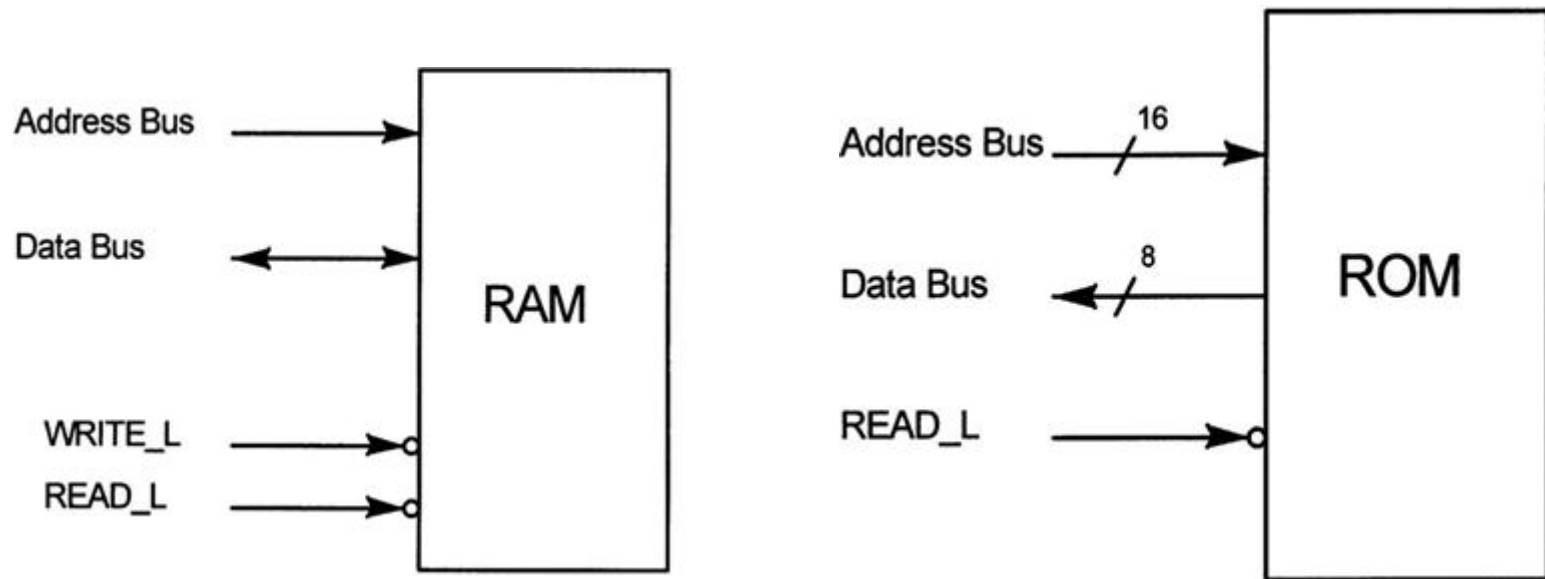

**READ\_L** is active low read enable  
**WRITE\_L** is active low write enable


# Memory Read Cycle

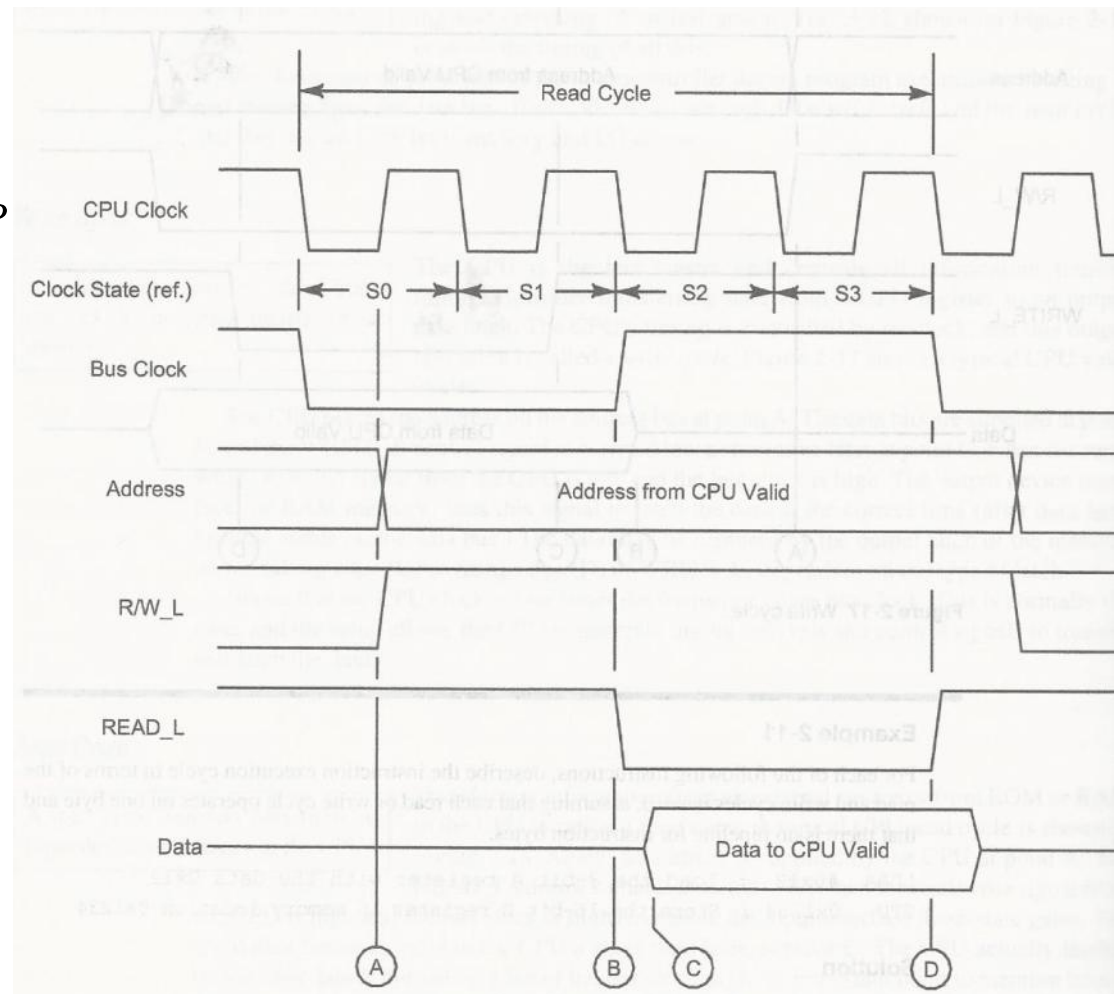- A. CPU put read address on the address bus and initiate R/W OP
- B. At next pos-edge of bus clock, CPU set `READ_L` control bit
- C. Data become available on the data bus shortly after
- D. On neg-edge pf bus cock CPU deassert `READ_L` signal, `RW_L` is also deasserted on next pos-edge of CPU clock




# Memory Write Cycle

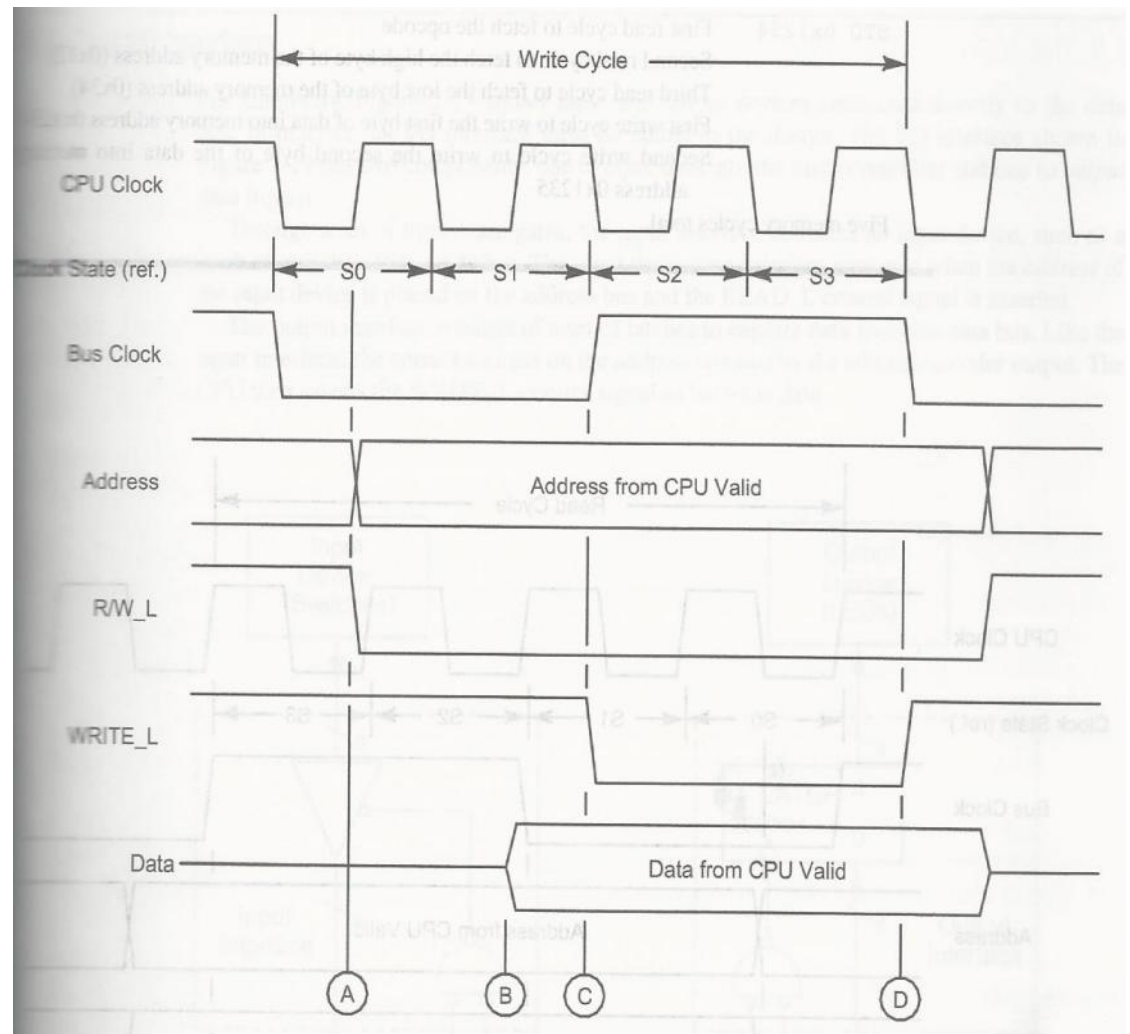
- A. CPU put read address on the address bus and initiate R/W OP
- B. At next pos-edge of CPU clock, CPU put data on the data bus
- C. On the next pos-edge of bus clock, CPU asserts `WRITE_L` control signal
- D. Data is written shortly after, and on neg-edge of bus clock CPU de-assert `WRITE_L` signal
- E. On next pos-edge of CPU clock CPU de-assert `RW_L` signal



# Pico Controller CPU

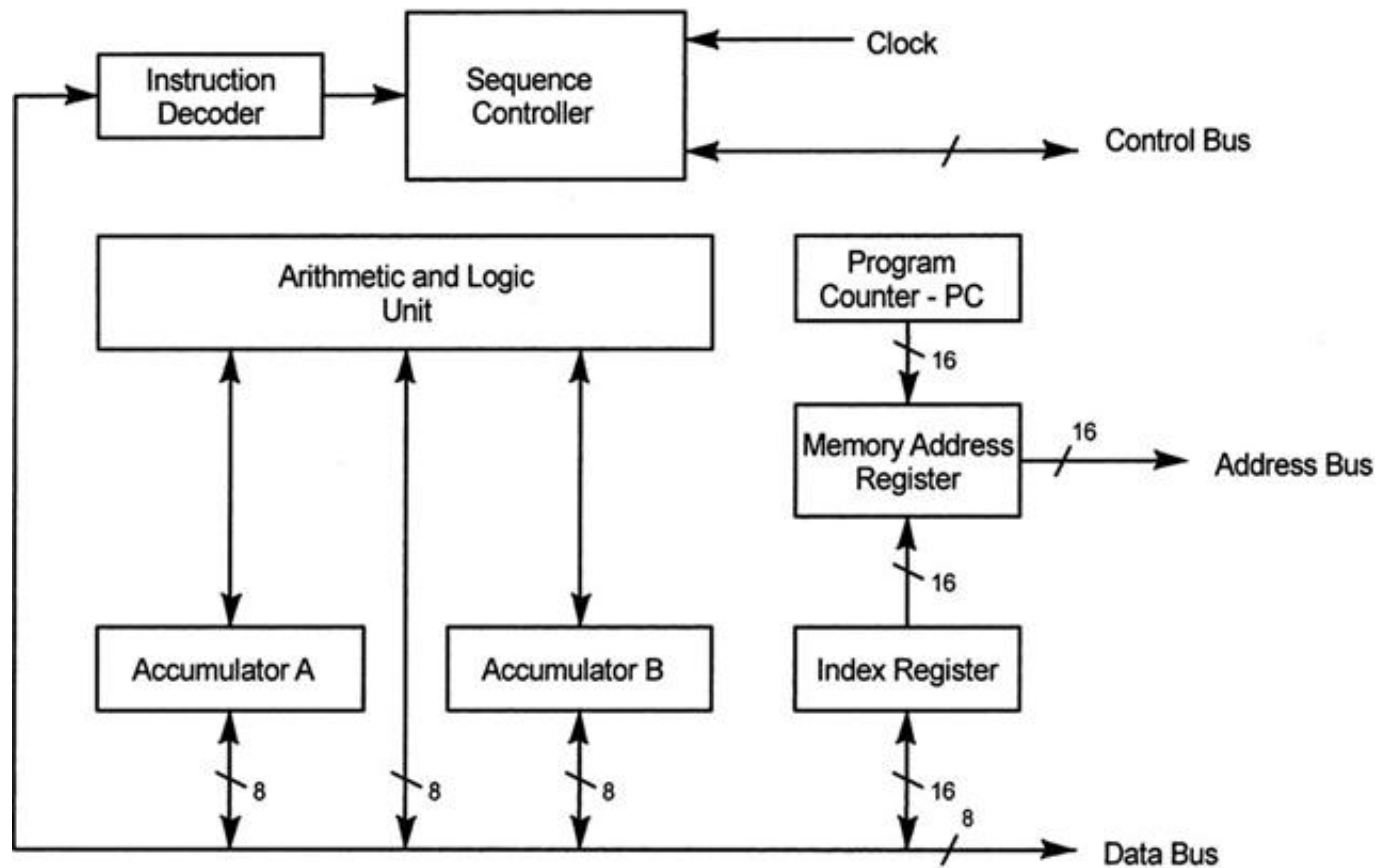

# Connecting RAM & ROM to the CPU

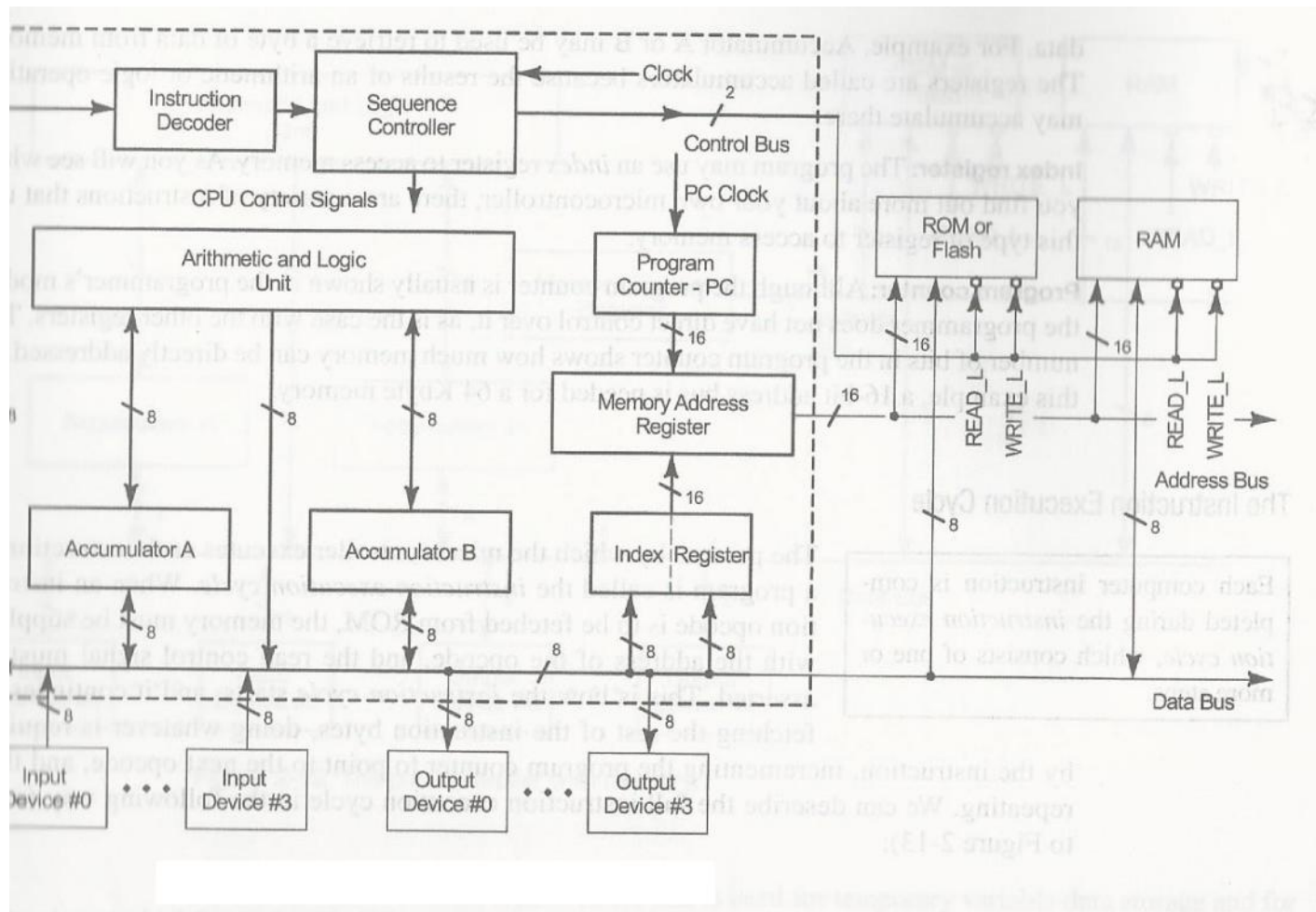

## Program in Computer Memory


	Operation Field		Comment Field	Addr	Contents
1	IN	1	$(A) \leftarrow (\text{Switches})$	0:	1010 0001
2	MOV		$(B) \leftarrow (A)$	1:	0100 0000
3	IN	1	$(A) \leftarrow (\text{Switches})$	2:	1010 0001
4	ADD		$(A) \leftarrow (A) + (B)$	3:	0010 0000
5	OUT	2	$(\text{LED}) \leftarrow (A)$	4:	1110 0010

# Instruction Register and Decoder


- **Instruction register**
  - Used to hold the computer instruction
- **Instruction decoder**
  - Logic circuit that decodes instruction
  - Asserts logic signals for each operation – example IN used as clock signal to latch data into the A register
  - Other logic signals not shown – decode OUT and IN operands to select devices



# Instruction Register and Decoder

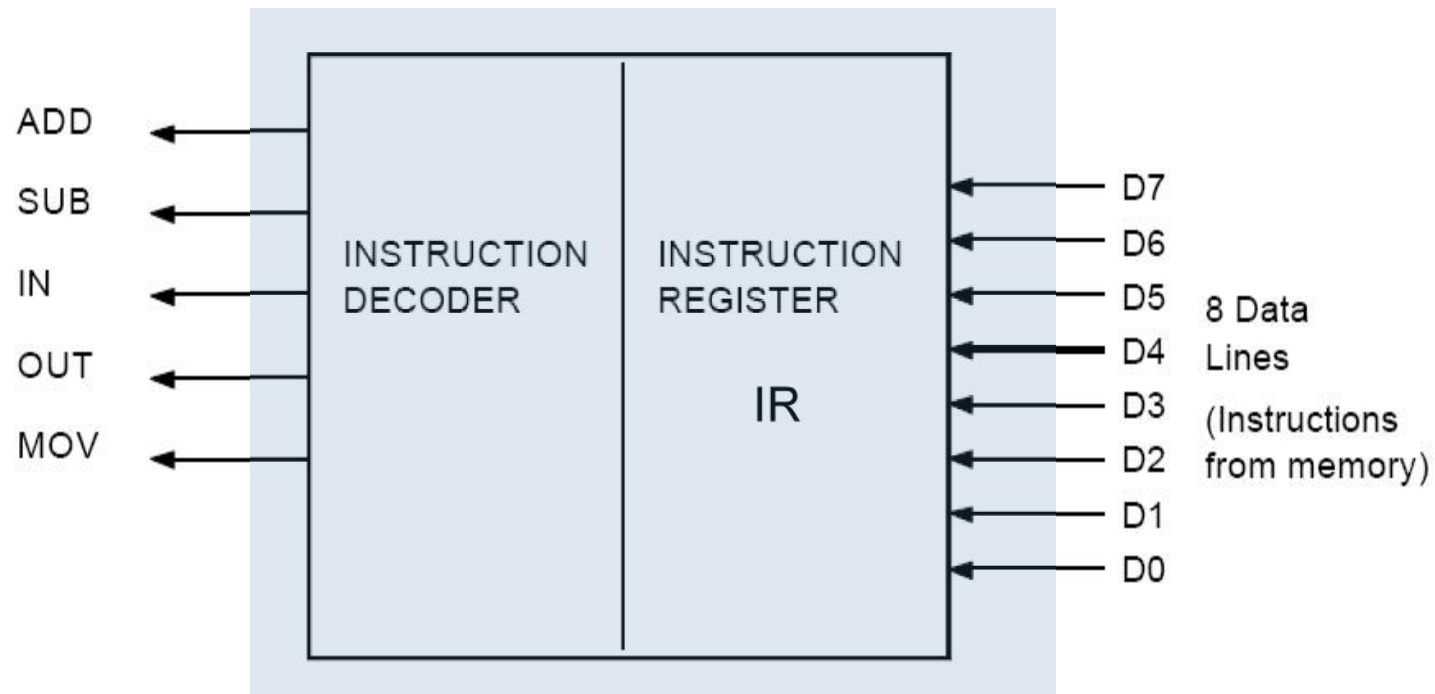


# Program Counter & Address Register

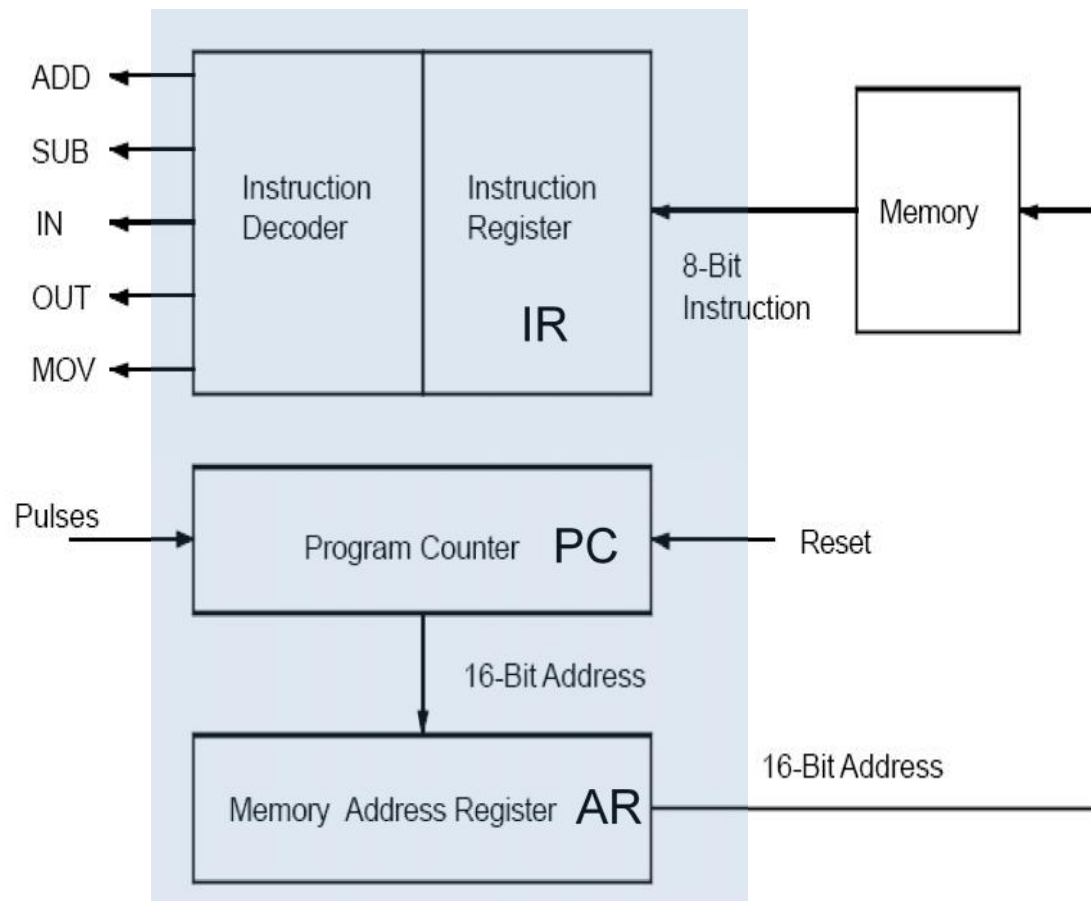

# IN Instruction Execution Cycle


- Need to start thinking about time it takes to execute instructions by considering the steps to execute an instruction
- Fetch instruction
  - Transfer contents of PC to Memory Address Register
  - Contents of addressed memory location transferred to Instruction Register (instruction decoded)
  - Instruction decoder asserts IN signal line
- Execution
  - Data in switches are transferred to A register
  - PC incremented to 0001
- Process repeated for next instruction

# CPU State Machine

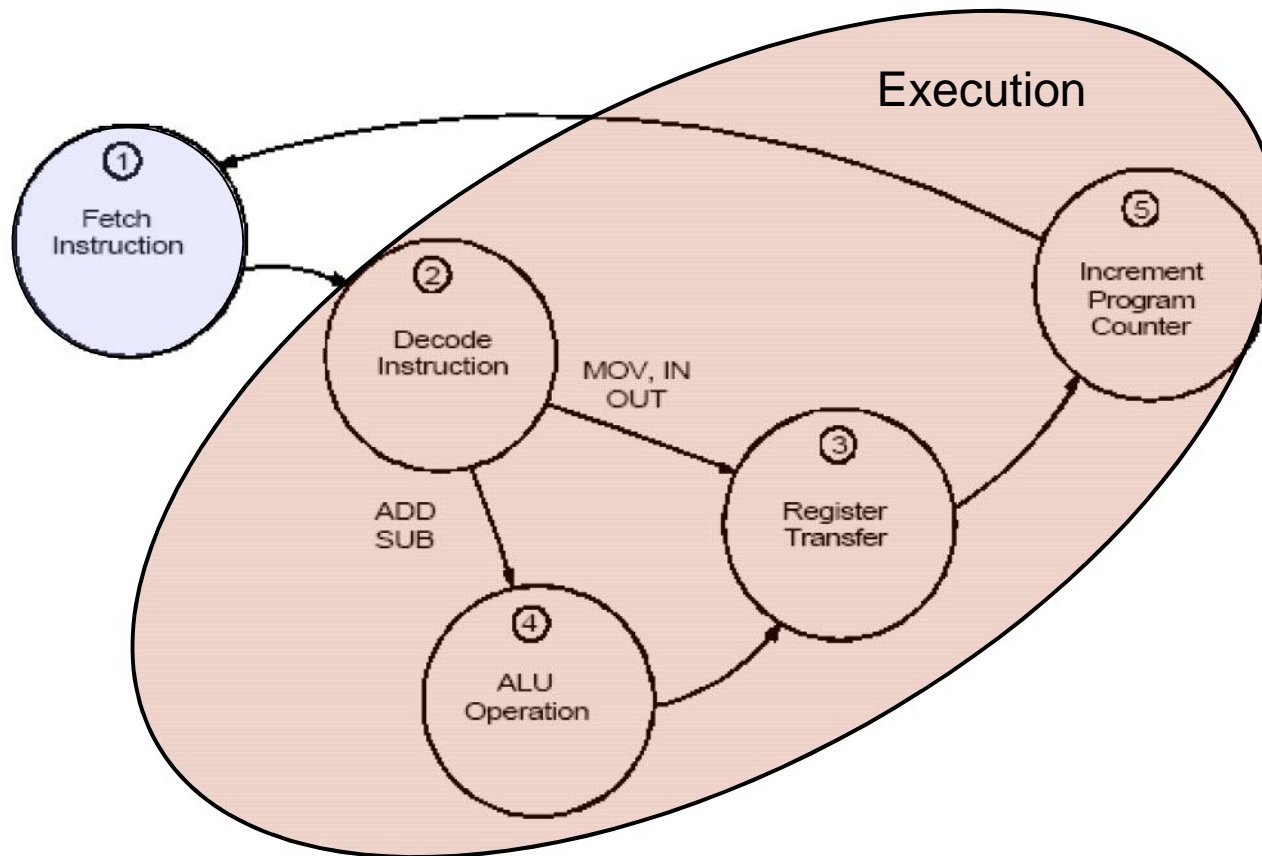

 
# CPU State Machine

- Break down instruction into small elements - states
  - Each element-state takes an amount of time
  - Allows time for event to occur
  - Event: Propagation of signals
- Sequence Controller:
  - Implements state machine
  - With Instruction decoder, generates control signals at appropriate time



 
# System Timing


- Sequential state machine operated by clock
- Consider 1 MHz clock –
- Pulse every 1  $\mu$ sec for each state



(a) Timing for the IN instruction.

 

(b) Timing for the ADD instruction.

 


## Program Execution Time

- Using 1 MHz clock, following table shows time to execute program

Instruction	Number of states
IN 1	4
MOV	4
IN 1	4
ADD	5
OUT 2	4
Total states	21 = 21 $\mu$ sec
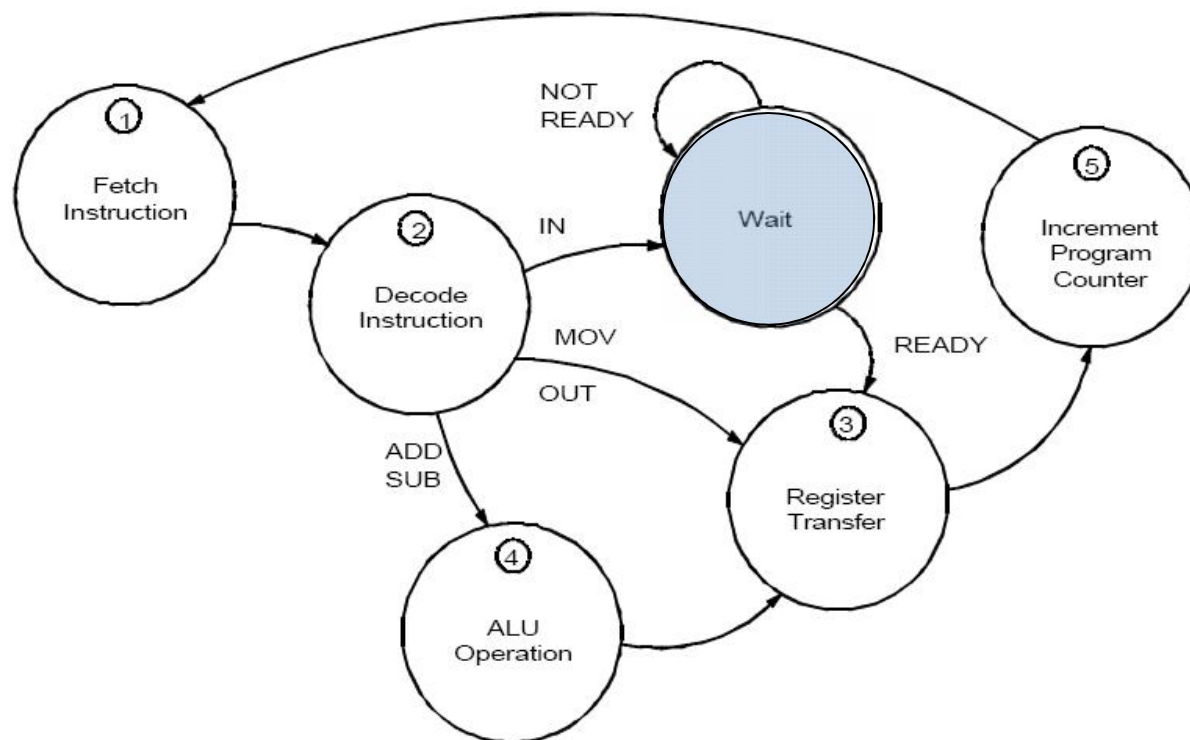
# I/O Synchronization and Wait States

- Wait state is used to synchronize with external event
  - Deals with slower devices (e.g. switches)




*Note: We can also add wait state for OUT instruction*



# What is missing

- Memory Reference instructions
  - Using different addressing modes
- Program control instructions
- Interrupts
- What else?!
- Will cover these later..

# Final Design

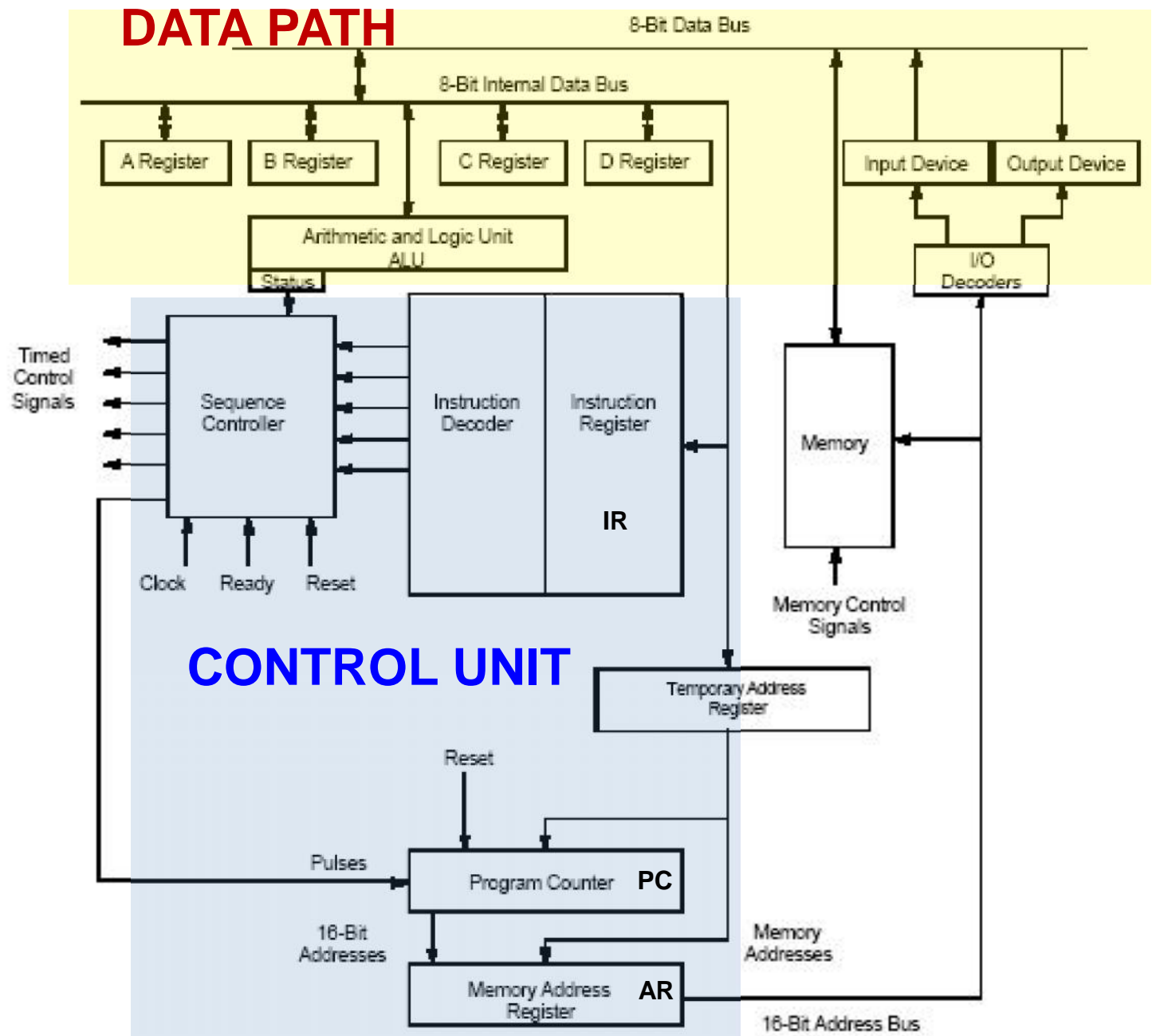

# References

- Fredrick M. Cady, Microcontrollers and Microcomputers: Principles of Software and Hardware Engineering – Chapter 1 & 2